

## EE386 Lab1

### Faculty of Engineering, University of Peradeniya

- (a) Implement the following weighted resistor digital to analog converter (Figure 1) in PSpice.
- (b) Explain the functionality of the DAC circuit.
- (c) Derive the expression for 3 bit DAC.
- (e) Vary the digital input from “000” to “111” and plot the curves  $V_0$ ,  $V_2$ ,  $V_4$ , and  $V_{DAC}$
- (f) Compute the analog voltages corresponding to digital inputs “011”, “101” and compare those results to the simulation results.

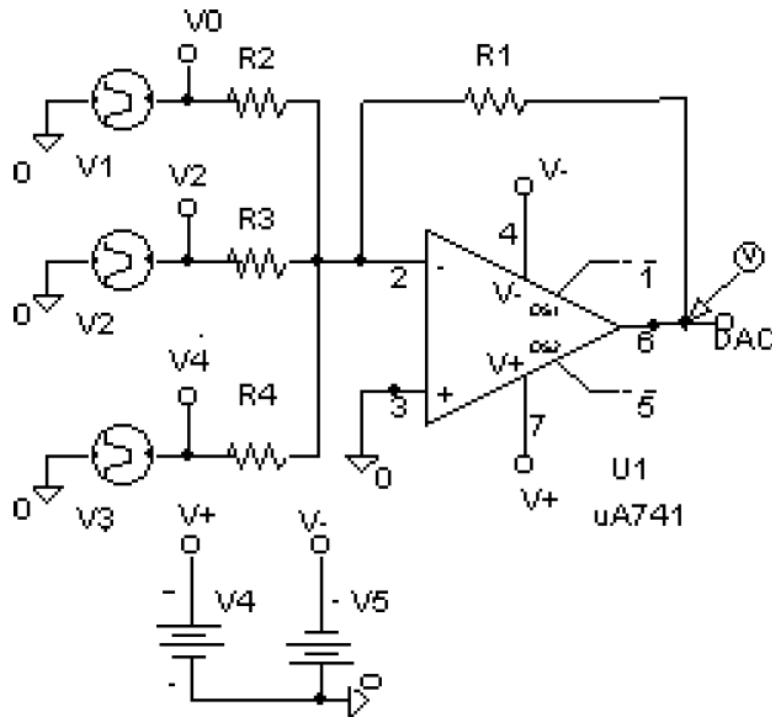


Figure 1. Weighted resistor digital to analog converter