

EE386 Lab2

Faculty of Engineering, University of Peradeniya

- (a) Implement the following R-2R ladder (Figure 1) digital to analog converter in PSpice.
- (b) Explain the functionality of the R-2R DAC circuit.
- (c) Derive the expression for a 3bit R-2R DAC.
- (d) Vary the digital input from “000” to “111” and plot the curves V_0 , V_2 , V_4 , and V_{DAC}
- (e) Compute the analog voltage corresponding to the bit combination to the digital input “011”, “101” and compare those results to the simulation results.

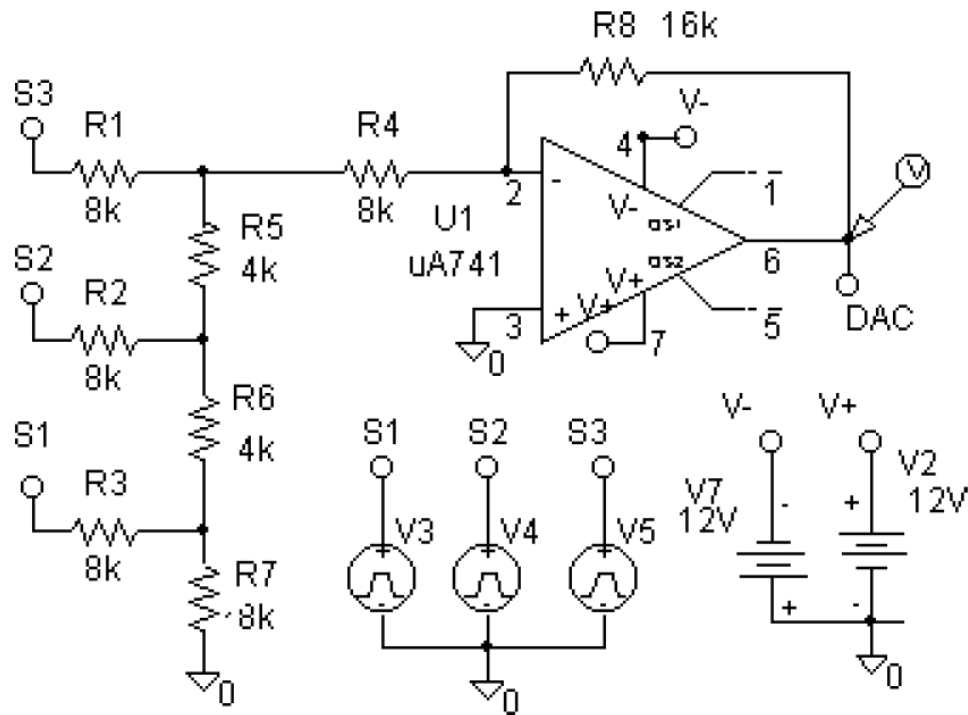


Figure 1. R-2R ladder digital to analog converter